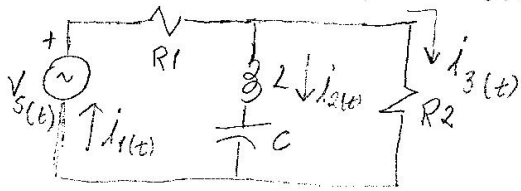


EJERCICIOS:

OBTENGA LA ECUACION DIFERENCIAL QUE RELACIONE $V_S(t)$ Y $i_3(t)$



a) ECUACIONES:

$$1) -V_S(t) + R_1 i_1(t) + R_2 i_3(t) = 0$$

$$2) -\frac{1}{C} \int i_2(t) dt - L \frac{d}{dt} i_2(t) + R_2 i_3(t) = 0$$

$$3) i_1(t) = i_2(t) + i_3(t)$$

SUST. (3) EN (1)

$$-V_S(t) + R_1 (i_2(t) + i_3(t)) + R_2 i_3(t) = 0 \Rightarrow$$

$$\Rightarrow i_2(t) = \frac{V_S(t)}{R_1} - \frac{(R_1 + R_2)}{R_1} i_3(t)$$

SUST EN (2)

$$-\frac{1}{C} \int \left[\frac{V_S(t)}{R_1} - \frac{R_1 + R_2}{R_1} i_3(t) \right] dt + \dots$$

$$-L \frac{d}{dt} \left\{ \frac{V_S(t)}{R_1} - \frac{R_1 + R_2}{R_1} i_3(t) \right\} + R_2 i_3(t) = 0$$

DERIVANDO Y REORDENANDO:

$$-\frac{V_S(t)}{R_1 C} + \frac{R_1 + R_2}{R_1 C} i_3'(t) - \frac{L}{R_1} \frac{d^2}{dt^2} V_S(t) + \dots$$

$$+ \frac{L \cdot (R_1 + R_2)}{R_1} \frac{d^2}{dt^2} i_3(t) + R_2 i_3'(t) = 0$$

ENTONCES:

$$\frac{d^2}{dt^2} i_3(t) + \left\{ \frac{1}{L} + \frac{R_2 \cdot R_1}{C(R_1 + R_2)} \right\} i_3'(t) = \frac{1}{R_1 + R_2} \frac{d}{dt} V_S(t) + \frac{V_S(t)}{LC(R_1 + R_2)}$$